

---

# Lecture23

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# Today's goal

---

- Read a netlist file and solve the DC problem.

r1 in out 100

r2 out 0 200

vin in 0 1

# Connectivity

---

- In principle, our problem is not very difficult. Application of KCL.
  - Key point: We should understand the connectivity of our elements.
  - Therefore, a table for the node names is required.
  - In the case of our example, we want to have 0 in out.
  - Instead of its name, a number is assigned.
- Then, our netlist can be written as

r1 2 3 100

r2 3 1 200

vin 2 1 1

# Read a netlist file

---

- Two elements
  - Resistor: Name starting with  $r$
  - Voltage source: Name starting with  $v$
  - Otherwise, an error occurs.
  - Again, a number is assigned to the element type (1 for voltage sources and 2 for resistors)
- Then, our netlist can be written as

2 2 3 100

2 3 1 200

1 2 1 1

# Implementation (1)

---

- Open the input file.

```
inputFileName = 'test.sp';
```

```
fileID = fopen(inputFileName, 'r');
```

```
if (fileID == -1)
```

```
    error(['I cannot open the file.']);
```

```
end
```

```
elementTable = [];
```

```
nodeTable = { '0' };
```

# Implementation (2)

---

- Read each line. Update nodeTable.

```
while ~feof(fileID)
    line = fgetl(fileID);
    C = strsplit(line);
    elementName = C{1};
    node1 = C{2};
    node2 = C{3};
    value = str2num(C{4});

    ind1 = find(strcmp(nodeTable,node1));
    if (isempty(ind1))
        nodeTable[size(nodeTable,1)+1,1] = node1;
    end
    ind2 = find(strcmp(nodeTable,node2));
    if (isempty(ind2))
        nodeTable[size(nodeTable,1)+1,1] = node2;
    end
```

# Implementation (3)

---

- Read each line. Update nodeTable.

```
ind1 = find(strcmp(nodeTable,node1));
ind2 = find(strcmp(nodeTable,node2));
switch elementName(1)
    case 'v'
        elementTable = cat(1,elementTable,[1 ind1 ind2 value]);
    case 'r'
        elementTable = cat(1,elementTable,[2 ind1 ind2 value]);
    otherwise
        error(['Only v and r are supported.']);
end
end
```

# Our example

---

- When it is processed, we have the following results.

```
>> SPICE
```

```
>> nodeTable
```

```
nodeTable =
```

```
    '0'
```

```
    'in'
```

```
    'out'
```

```
>> elementTable
```

```
elementTable =
```

```
    2    2    3   100
```

```
    2    3    1   200
```

```
    1    2    1     1
```



# Unknown variables

---

- Four unknown variables for each element
  - Current for the terminal 1
  - Current for the terminal 2
  - Voltage for the terminal 1
  - Voltage for the terminal 2
- How many unknown variables?
  - (# of elements) times (4)
  - Anything else?
  - Additionally, (# of nodes) for the node voltages.
  - In the case of our example, we have 15 unknown variables.

# Resistor

---

- Four equations for each resistor

- Ohm's law

$$i1 - \frac{v1 - v2}{R} = 0$$

- (Current for the terminal 1) + (Current for the terminal 2) = 0

$$i1 + i2 = 0$$

- (Voltage for the terminal 1) – (Connected node voltage) = 0

- (Voltage for the terminal 2) – (Connected node voltage) = 0

- Also the terminal current is added to the node equation.

# Voltage source

---

- Four equations for each resistor
  - Voltage across the voltage source
$$v1 - v2 - v_{source} = 0$$
  - (Current for the terminal 1) + (Current for the terminal 2) = 0
$$i1 + i2 = 0$$
  - (Voltage for the terminal 1) – (Connected node voltage) = 0
  - (Voltage for the terminal 2) – (Connected node voltage) = 0
- Also the terminal current is added to the node equation.

# Implementation (4)

---

- Prepare some quantities.

```
nElement = size(elementTable,1);
```

```
nodeOffset = nElement * 4;
```

```
nNode = size(nodeTable,1);
```

```
nTotal = nodeOffset+nNode;
```

```
Jaco = sparse(nTotal,nTotal);
```

```
res = zeros(nTotal,1);
```

```
sol = zeros(nTotal,1);
```

# Implementation (5)

---

- Consider each element.

```
for ii = 1:nElement
    elementOffset = (ii-1)*4;
    type = elementTable(ii,1);
    ind1 = elementTable(ii,2);
    ind2 = elementTable(ii,3);
    value = elementTable(ii,4);
```

# Implementation (6)

---

- Ohm's law / voltage difference

```
% Equation 1
switch type
    case 1
        res(elementOffset+1) = sol(elementOffset+3) - sol(elementOffset+4)
- value;
        Jaco(elementOffset+1,elementOffset+1:elementOffset+4) = [0 0 1 -
1];
    case 2
        res(elementOffset+1) = sol(elementOffset+1) -
(sol(elementOffset+3)-sol(elementOffset+4))/value;
        Jaco(elementOffset+1,elementOffset+1:elementOffset+4) = [1 0 -
1/value 1/value];
    otherwise
        error(['Only v and r are supported.']);
end
```

# Implementation (7)

---

- Other equations

```
% Equation 2
```

```
res(elementOffset+2) = sol(elementOffset+1) + sol(elementOffset+2);
```

```
Jaco(elementOffset+2,elementOffset+1:elementOffset+4) = [1 1 0 0];
```

```
% Equation 3
```

```
res(elementOffset+3) = sol(elementOffset+3) - sol(nodeOffset+ind1);
```

```
Jaco(elementOffset+3,elementOffset+1:elementOffset+4) = [0 0 1 0];
```

```
Jaco(elementOffset+3,nodeOffset+ind1) = -1;
```

```
% Equation 4
```

```
res(elementOffset+4) = sol(elementOffset+4) - sol(nodeOffset+ind2);
```

```
Jaco(elementOffset+4,elementOffset+1:elementOffset+4) = [0 0 0 1];
```

```
Jaco(elementOffset+4,nodeOffset+ind2) = -1;
```

# Implementation (8)

---

- KCL and all other stuffs

```
% Node equation 1
res(nodeOffset+ind1) = res(nodeOffset+ind1) + sol(elementOffset+1);
Jaco(nodeOffset+ind1,elementOffset+1) = Jaco(nodeOffset+ind1,elementOffset+1) +
1;

% Node equation 2
res(nodeOffset+ind2) = res(nodeOffset+ind2) + sol(elementOffset+2);
Jaco(nodeOffset+ind2,elementOffset+2) = Jaco(nodeOffset+ind2,elementOffset+2) +
1;

end


% Ground
res(nodeOffset+1) = sol(nodeOffset+1);
Jaco(nodeOffset+1,:) = 0;
Jaco(nodeOffset+1,nodeOffset+1) = 1;

sol = Jaco \ (-res);
```



# Jacobian sparsity pattern

- We can read it.

 

# Solution vector

---

- Check the solution.

```
>> sol
```

```
sol =
```

```
  0.0033  
 -0.0033  
  1.0000  
  0.6667  
  0.0033  
 -0.0033  
  0.6667  
  0  
 -0.0033  
  0.0033  
  1.0000  
  0  
  0  
  1.0000  
  0.6667
```